

THE INSTITUTION OF ENGINEERS, SRI LANKA
IESL ENGINEERING COURSE

PART III EXAMINATION—JUNE 2010
309 ELECTRONICS

Instructions: This question paper contains eight questions in 5 pages. Answer **five** questions **only**. Tentative mark allocation for each part is shown in brackets for guidance only. **Time:** Three hours.

- Q1. (a) List commonly used filter transfer functions and their characteristics. [4 marks]
 (b) A second order stage is shown in Figure 1, where v_I is the input voltage and v_O is the output voltage. Show that its transfer function is [6 marks]

$$A(s) = - \frac{\frac{R_2}{R_1}}{1 + C_1 \left(R_2 + R_3 + \frac{R_2 R_3}{R_1} \right) s + C_1 C_2 R_2 R_3 s^2}$$

 


Figure 1: Circuit for Q1b.

- (c) Use the second order stage in Figure 1 and other circuitry as necessary to design a third-order unity-gain Butterworth low-pass filter with a corner frequency of $f_C = 50$ kHz. You may use only 22 pF and 1 nF capacitors. Butterworth coefficients for the third-order filter are [10 marks]

| Order n | Stage i | a_i | b_i |
|-----------|-----------|--------|--------|
| 3 | 1 | 1.0000 | 0.0000 |
| | 2 | 1.0000 | 1.0000 |

for a transfer function of a stage of the form

$$A_i(s) = \frac{A_o}{1 + a_i s + b_i s^2}$$

- Q2. (a) Sketch the circuit diagrams of the non-inverting and inverting bistable multivibrators along with their voltage transfer characteristics. [6 marks]
- (b) Sketch the circuit diagram of a free-running triangular waveform generator. [4 marks]
- (c) Figure 2 shows a one shot circuit. The operational amplifier is supplied with voltage levels L_+ and L_- . In the stable state, $v_O = L_+$, $v_A = 0$, and $v_B = -V_{ref}$. The circuit is triggered by applying a positive input pulse of height greater than V_{ref} . Assume that $C_1 R_1 \ll CR$. [10 marks]
- Sketch the waveforms v_A , and v_O along with the trigger pulse.
 - What is the width T of the pulse generated at the output?
 - How would you control the pulse width T ?

 


Figure 2: Circuit for Q2c.

- Q3. (a) Figure 3 shows a simple common-emitter amplifier. $V_{CC} = 20\text{ V}$ and $R_C = 140\ \Omega$. [6 marks]
- If there are two transistors with total power dissipation 0.4 W, and 0.6 W, what would you select?
 - In regard to the transistor power dissipation, how would you accommodate a substantial change in the ambient temperature without replacing the transistor?

 


Figure 3: Circuit for Q3a.

- (b) A class B power amplifier stage is to be designed to deliver an average power of 20 W to an 8- Ω load. The power supply voltage V_{CC} is to be 5 V greater than the peak output voltage. [8 marks]
- Compute the average power drawn from each supply.
 - Compute the power conversion efficiency and compare with the maximum efficiency.
 - Determine the maximum power each transistor should be able to dissipate.

- iv. Why is the supply voltage selected to be 5 V greater than the peak output voltage?
- (c) Figure 4 shows an output stage. Identify its type and provide a short-circuit protection mechanism for this output stage. [6 marks]

 


Figure 4: Circuit for Q3c.

- Q4. (a) Compare unregulated and regulated power supplies paying special attention to the operating principle of regulated power supplies. [6 marks]
- (b) A regulator circuit is shown in Figure 5 with $V_{ref} = 7.15\text{ V}$. Give a step-by-step explanation of its operation and compute its output voltage and maximum current. [8 marks]
- (c) The circuit in Figure 5 does not have over voltage protection. Provide an over voltage crowbar protection and explain what happens when the output exceeds the maximum voltage. [6 marks]

 


Figure 5: Circuit for Q4b.

- Q5. (a) Describe the characteristics and applications of the SCR, diac, triac, and UJT. Show sketches of I - V characteristics. [8 marks]
- (b) The triac in the power controller circuit shown in Figure 6 has an anode-cathode voltage drop of 1 V when it is conducting. If $R_L = 30\Omega$, find the rms value of v_{in} that is necessary if it is required to deliver an average power of 100 W to R_L when the firing angle is 45° ? [6 marks]

 


Figure 6: Circuit for Q5b.

- (c) An SCR with a forward break over voltage $V_{BR(F)} = 10$ V is supplied by a sawtooth waveform of peak amplitude 30 V (Figure 7) through a $50\text{-}\Omega$ resistor. When conducting, the anode-cathode voltage drop of the SCR is 1 V. Find the average current in R_L . [6 marks]

 


Figure 7: Circuit for Q5c.

- Q6.** (a) A 32×6 ROM converts a six-bit binary number to its corresponding two-digit binary-coded decimal (BCD) number. Note that to represent six-bit binary numbers as BCD, at least seven bits as required. [6 marks]
Design the system and specify the truth-table for the ROM. [8 marks]
- (b) Consider the following Boolean functions:

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$

Simplify, and implement these using a PAL. Show the PAL programming table and the fuse map.

- (c) FPGAs are known to be very versatile and widely used. Describe the reason for this trend by mentioning the advantages of FPGAs. [6 marks]

- Q7.** (a) Consider the following signal

$$v(t) = 5 \sin(2\pi f) + 5 \text{ V.}$$

where $f = 10$ kHz. It is sampled at $f_s = 12$ kHz and each sample is quantized into 5 bits. [8 marks]

- Sketch two cycles of the input waveform along with the waveform reconstructed from the quantized samples.
 - How would you solve the main problem in the aforementioned process?
 - If the sampled voltage value needs to be wrong by no more than 0.5 mV, how many bits per sample would be required?
- (b) Explain how dual-slope integration ADCs avoid some problems in single-slope integration ADCs. [4 marks]
- (c) An 8-bit successive approximation register ADC with a full-range input voltage of 10 V is presented with an input voltage of 7.1 V. List the sequence of digital outputs until the output settles down. [8 marks]

- Q8.** (a) Sketch a block diagram of a computer clearly indicating the data and control paths, and describe the operation. [6 marks]
- (b) Using a sketch show how a 2048-byte memory can be constructed using 128×8 -bit chips. Clearly indicate the number of address lines, and how they are connected to the chips. [6 marks]
- (c) Arithmetic and logic operations in a microprocessor are handled by the ALU which is a combinational circuit. Using sketches of these circuits show how the operations, AND, addition, and subtraction are done in an ALU. [8 marks]